

7447 BCD-Seven Segment Display decoder

Shaik Mohisena Tabassum
Roll No: FWC22279
shaikmohisena123@gmail.com

I. ABSTRACT

The document shows how to use the 7447 BCD-Seven Segment Display decoder to learn boolean logic.

II. COMPONENTS

The required components list is given in Table: I. The pin diagram of the seven segment display is shown in Fig.1. The pin diagram of IC 7447 is shown in Fig.2

Components	Value	Quantity
Seven Segment Display		1
IC	7447	1
Arduino	UNO	1
Jumper Wires		10
Breadboard		1

TABLE I

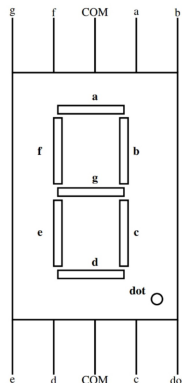


Fig. 1.

III. PROCEDURE

- 1) Make the connections between 7447 and Seven segment display as per the Table: II.
- 2) Make the connections between Arduino and 7447 as per the Table: III.

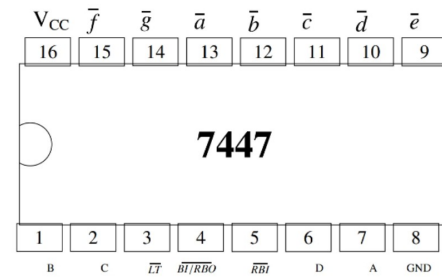


Fig. 2.

7447	a-bar	b-bar	c-bar	d-bar	e-bar	f-bar	g-bar
Display	a	b	c	d	e	f	g

TABLE II

- 3) The truth table for the increment decoder is shown in Table IV.
- 4) Run the code. And observe the output in the display as in Fig.3.

7447	D	C	B	A
Arduino	5	4	3	2

TABLE III

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE IV

IV. RESULTS

Download the code given in the link below and execute them to see the output as shown in Fig.3 by observing in seven segment display.

<https://github.com/Tabassum4930/FWC-1/blob/main/Ide/7447/code.cpp>

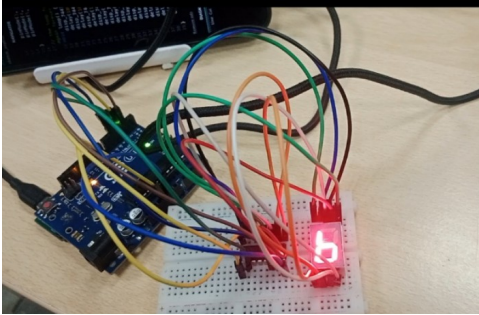


Fig. 3.

V. CONCLUSION

Therefore, it is an essential component in the experimentation of digital circuits.