

Platformio Assignment

Shaik Mohisena Tabassum
Roll No: FWC22279
shaikmohisena123@gmail.com

I. ABSTRACT

In the circuit as shown in Fig.1, the present value of Z is 1. Neglecting the delay in the combinational circuit, the values of S and Z , respectively, after the application of the clock will be

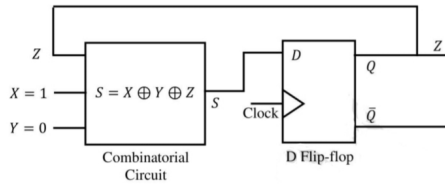


Fig. 1.

II. COMPONENTS

The required components list is given in Table: I. Flip-flop IC 7474 diagram is shown in Fig.2.

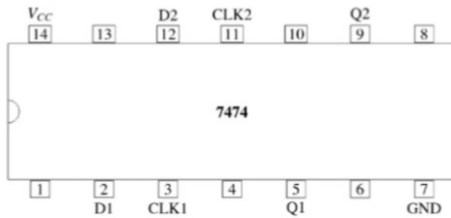


Fig. 2.

Components	Value	Quantity
IC	7474	1
LEDs		1
Arduino	UNO	1
Jumper Wires		10
Breadboard		1

TABLE I

III. PROCEDURE

Make the connections between Arduino and 7474 as per the Table: II.

Arduino Pin	7474
D5	2
D6	3
D4	5
5 V	14
gnd	7

TABLE II

IV. RESULTS

Download the code given in the link below and execute them to see the output as shown in Fig.2 by placing the LED at the output pin of 7474 IC.

https://github.com/Tabassum4930/FWC_1/blob/main/Platformio/code.cpp

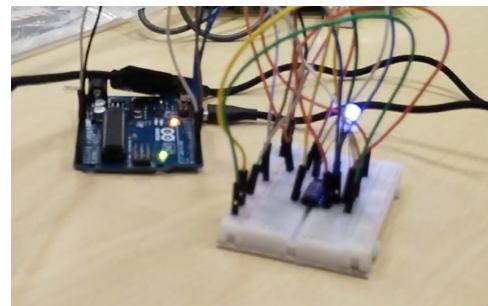


Fig. 3.

V. CONCLUSION

The D-Flip Flop is a good application in order to use it for registers. Here, the sequential circuit is combined with the combinational circuit of XOR gates to get the output. Therefore, we can design several circuits and can be implemented using Arduino and Platformio.